

Lele

Outline:

- Simple harmonic motion
- RLC circuits

Last time:

Variation of parameters: $y'' + a_1 y' + a_2 y = Q(x)$, homog. y_1, y_2

$y_p = u_1 y_1 + u_2 y_2$, where u_1, u_2 are functions and

$$u_1' y_1 + u_2' y_2 = 0$$


$$u_1' y_1' + u_2' y_2' = Q(x)$$

Note, our equation had $a_2 = 1$, otherwise need $\frac{Q(x)}{a_2}$ here.

Reduction of order: possible to find 1 additional linearly ind. sol if we already know $n-1$ linearly ind. sol. for order n linear ODE

This time:

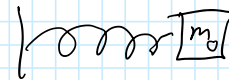- Recall we studied simple harmonic motion earlier




$$m_0 \ddot{x} + 2m_0 r \dot{x} + m_0 \omega_0^2 x = m_0 f(t) \Rightarrow \ddot{x} + 2r \dot{x} + \omega_0^2 x = f(t)$$

coefficient of resistance \uparrow
 $\omega_0 \sim$ natural (undamped) frequency

Char. eq. $m^2 + 2rm + \omega_0^2 = 0$
 $m = -r \pm \sqrt{r^2 - \omega_0^2}$

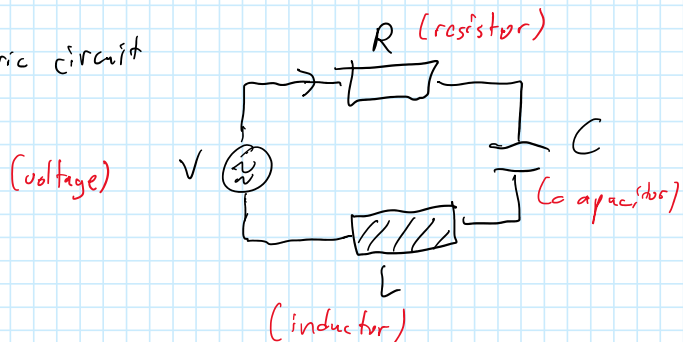- Let's consider a simple RLC electric circuit



Physics: $I(t) = \text{current}$ $L \dot{I}_L = V_L$ $L \ddot{I}_L = \dot{V}_L$
 $V(t) = \text{voltage difference}$ $C \dot{V}_C = I_C$ $\frac{I_C}{C} = \dot{V}_C$
 $V_R = R I_R$ (Ohm's Law) $\dot{V}_R = R \dot{I}_R$

Kirchhoff's 1st Law: $I_L = I_C = I_R$

Kirchhoff's 2nd Law: $V_R + V_L + V_C = V$

$\dot{V}_R + \dot{V}_L + \dot{V}_C = \dot{V}$

$R \dot{I} + L \ddot{I} + \frac{I}{C} = \dot{V}$

Note $L \geq 0$
 $C \geq 0$
 $R \geq 0$

2nd order ODE: $L \ddot{I} + R \dot{I} + \frac{1}{C} I = \dot{V}$

Let $\eta = \frac{R}{2L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

$\ddot{I} + \frac{R}{L} \dot{I} + \frac{1}{LC} I = \frac{\dot{V}}{L}$

$\ddot{I} + 2\eta \dot{I} + \omega_0^2 I = \frac{\dot{V}}{L}$

harmonic motion
 $\ddot{x} + 2r \dot{x} + \omega_0^2 x = f(t)$


The RLC system and forced damped harmonic motion have the same behavior.

η and r are damping terms, determined by friction, or by the resistor & inductor.

What if $\eta = 0$ ($r = 0$) i.e. no damping

$\ddot{x} + \omega_0^2 x = 0$

Then $x_c = A \cos(\omega_0 t) + B \sin(\omega_0 t) = \text{Re} (A e^{i\omega_0 t} - i B e^{i\omega_0 t})$
 $= \text{Re} [(A - Bi) e^{i\omega_0 t}] = \text{Re} (\sqrt{A^2 + B^2} e^{(-\tan^{-1} \frac{B}{A}) i} e^{i\omega_0 t})$

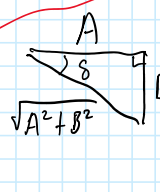 $\tan \delta = \frac{-B}{A}$
 $\delta = -\tan^{-1} \frac{B}{A}$

$$\sqrt{A^2+B^2} \quad \delta = -\tan^{-1} \frac{B}{A}$$


$$= \sqrt{A^2+B^2} \cdot \operatorname{Re} \left(e^{i(\omega_0 t - \tan^{-1} \frac{B}{A})} \right)$$

$$= \sqrt{A^2+B^2} \cdot \cos \left(\omega_0 t - \tan^{-1} \frac{B}{A} \right)$$

$$= C \cdot \cos(\omega_0 t - \delta), \quad \delta \text{ is a phase shift}$$

C is amplitude

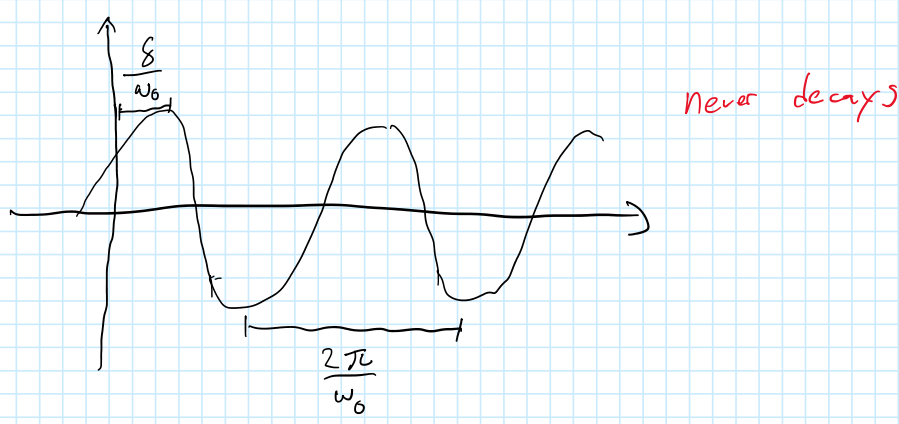ω_0 is the resonance (or natural undamped) angular frequency (in radians)
 (or $\frac{\omega_0}{2\pi}$ is the resonance frequency in cycles/sec)



What if $\eta > 0$ ($r > 0$)

$$\ddot{x} + 2\eta \dot{x} + \omega_0^2 x = 0$$

Char. eq. $m^2 + 2\eta m + \omega_0^2 = 0$

$$m = -\eta \pm \sqrt{\eta^2 - \omega_0^2}$$

3 cases:

$\eta > \omega_0$
 2 distinct real roots $m_1, m_2 < 0$
 $x_c = c_1 e^{m_1 t} + c_2 e^{m_2 t}$

$\eta = \omega_0$
 1 distinct real root $m = -\eta$
 $x_c = (c_1 + c_2 t) e^{-\eta t}$

$\eta < \omega_0$
 2 conjugate complex roots $m_1, m_2 = -\eta \pm \beta i$
 $x_c = c_1 e^{-\eta t} \cos(\beta t) + c_2 e^{-\eta t} \sin(\beta t)$
 $= A e^{-\eta t} \cos(\beta t - \delta)$




over damping



critical damping

$$= A e^{-\eta t} \cos(Bt - \delta)$$

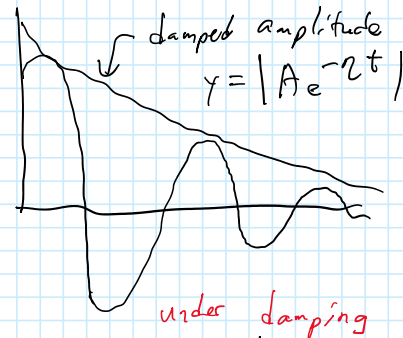

damped amplitude $\gamma = |A e^{-\eta t}|$

under damping

damped period $\tau = \frac{2\pi}{\omega} = \frac{2\pi}{\sqrt{\omega_0^2 - \eta^2}}$

The homogeneous soln always decays to 0 exponentially fast if there is damping.

Known as transient motion because always decays

Forcing function $\ddot{x} + 2\eta \dot{x} + \omega_0^2 x = f(t)$

- Suppose constant force $f(t) = 1$

Method of undetermined coeff

$$\left. \begin{array}{l} x_p = c_1 \\ \dot{x}_p = 0 \\ \ddot{x}_p = 0 \end{array} \right\} \left. \begin{array}{l} \omega_0^2 c_1 = 1 \\ c_1 = \frac{1}{\omega_0^2} \end{array} \right\} x_p = \frac{1}{\omega_0^2}$$

- Suppose periodic forcing term $f(t) = \cos(\omega t)$

Solve by using complex numbers $\cos(\omega t) = \text{Re}(e^{i\omega t})$

$$x_p = k e^{i\omega t} \rightarrow -\omega^2 k e^{i\omega t} + 2i\omega\eta k e^{i\omega t} + \omega_0^2 k e^{i\omega t} = e^{i\omega t}$$

$$-\omega^2 k + 2i\omega\eta k + \omega_0^2 k = 1$$

$$k = \frac{1}{(\omega_0^2 - \omega^2) + i(2\omega\eta)}$$

$$x_p = \frac{1}{(\omega_0^2 - \omega^2) + i(2\omega\eta)} e^{i\omega t}$$

If no damping: $\ddot{x} + \omega_0^2 x = Fe^{i\omega t}$ (or $\cos \omega_0 t$)

$m = \pm i\omega_0$, homog. soln. $e^{-i\omega_0 t}, e^{i\omega_0 t}$

Then $x_p = k_1 e^{i\omega_0 t} + k_2 t e^{i\omega_0 t}$

$\dot{x}_p = i\omega_0 k_1 e^{i\omega_0 t} + i\omega_0 k_2 t e^{i\omega_0 t} + k_2 e^{i\omega_0 t}$

$\ddot{x}_p = -\omega_0^2 k_1 e^{i\omega_0 t} + 2i\omega_0 k_2 e^{i\omega_0 t} - \omega_0^2 k_2 t e^{i\omega_0 t}$

red terms cancel out when substituted into $\ddot{x} + \omega_0^2 x = Fe^{i\omega t}$

$\Rightarrow 2i\omega_0 k_2 e^{i\omega_0 t} = Fe^{i\omega_0 t}$

$2i\omega_0 k_2 = F \Rightarrow k_2 = \frac{F}{2i\omega_0} = \frac{-iF}{2\omega_0}$

$x_p = \frac{-iF}{2\omega_0} t e^{i\omega_0 t} = \frac{-iF}{2\omega_0} t \cdot (\cos(\omega_0 t) + i \sin(\omega_0 t))$

$\text{Re}(x_p) = \frac{F}{2\omega_0} t \cdot \sin(\omega_0 t) \leftarrow \text{blows up as } t \rightarrow \infty$

With damping: $\ddot{x} + 2\eta\dot{x} + \omega_0^2 x = Fe^{i\omega t}$ (or $\cos \omega_0 t$)

$(\omega = \omega_0) \quad x_p = \frac{F}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2}} \cdot \cos(\omega t - \alpha) = \frac{F}{2\omega_0\eta} \cdot \cos(\omega_0 t - \alpha)$

So amplitude $\frac{F}{2\omega_0\eta}$. If damping is small, this blows up, but not all the way to infinity

Does this maximize amplitude?

No. We want $\frac{F}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2}}$ to be large, so equivalently

maximize $g_1(\omega) = \frac{1}{(\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2}$ or equivalently,

minimize $g_2(\omega) = (\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2 = (\omega_0^2 - \omega^2)^2 + 4\omega^2\eta^2$

$g_2'(\omega) = 2(\omega_0^2 - \omega^2) \cdot -2\omega + 8\omega\eta^2$

$\Rightarrow -\omega(\omega_0^2 + \omega^2) + 2\omega\eta^2 = 0$

$-\omega_0^2 + \omega^2 + 2\eta^2 = 0$

$\omega^2 = \omega_0^2 - 2\eta^2$

$\omega = \sqrt{\omega_0^2 - 2\eta^2}, \quad \omega_0^2 > 2\eta^2.$


Thus, if $\omega = \sqrt{\omega_0^2 - 2\eta^2}$, $A_{\max} = \frac{F}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2}}$

$$\begin{aligned}
 \text{Thus, if } \omega &= \sqrt{\omega_0^2 - 2\eta^2}, \quad A_{\max} = \frac{F}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\omega\eta)^2}} \\
 &= \frac{F}{\sqrt{[\omega_0^2 - (\omega_0^2 - 2\eta^2)]^2 + 4\eta^2(\omega_0^2 - 2\eta^2)}} \\
 &= \frac{F}{\sqrt{(2\eta^2)^2 + 4\eta^2(\omega_0^2 - 2\eta^2)}} \\
 &= \frac{F}{\sqrt{4\eta^4 + 4\eta^2\omega_0^2 - 8\eta^4}} \\
 &= \frac{F}{\sqrt{4\eta^2\omega_0^2 - 4\eta^4}} = \frac{F}{2\eta\sqrt{\omega_0^2 - \eta^2}}
 \end{aligned}$$

We then say that the forcing function $e^{i\omega t}$ is in resonance with the system. It doesn't blow up to infinity, but still gets very large.

Note that if η is small, $A_{\max} \approx \frac{F}{2\eta\omega_0}$, which makes sense because when η is small, the optimal $\omega = \sqrt{\omega_0^2 - 2\eta^2} \approx \omega_0$.

Ex.

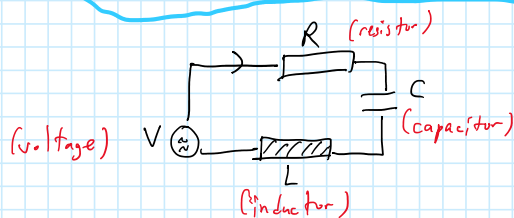

Suppose we have a simple circuit with a fixed voltage source $V = 9$ volts, a resistor with $R = 3$ ohms, inductor $L = 1$ henry, capacitor $C = 0.5$ farads.

What is the current in amps moving across the system at time t .

$$L\ddot{I} + R\dot{I} + \frac{1}{C}I = \dot{V}$$

$$\ddot{I} + 3\dot{I} + 2I = 0$$

Char. eq. $m^2 + 3m + 2 = 0$

$$m = -1, -2$$

Sol. e^{-t}, e^{-2t}

$$\Rightarrow I = c_1 e^{-t} + c_2 e^{-2t} \rightarrow 0 \text{ as } t \rightarrow \infty$$

What if the voltage is varying with $V(t) = \sin(t)$?

What if the voltage is varying with $V(t) = \sin(t)$?

$$\ddot{I} + 3\dot{I} + 2I = \cos t = \operatorname{Re}(e^{it})$$

homog. soln. $I_c = c_1 e^{-t} + c_2 e^{-2t}$

Use method of undetermined coed. to find particular soln.

$$I_p = k e^{it}, \quad \dot{I}_p = i k e^{it}, \quad \ddot{I}_p = -k e^{it}$$

$$-k e^{it} + 3i k e^{it} + 2k e^{it} = e^{it}$$

$$k(-1 + 3i + 2) = 1$$

$$k = \frac{1}{1 + 3i} = \frac{1 - 3i}{10}$$

$$I_p = \frac{1 - 3i}{10} e^{it} = \frac{1 - 3i}{10} (\cos t + i \sin t)$$

$$\operatorname{Re}(I_p) = \frac{1}{10} \cos t + \frac{3}{10} \sin t$$

What is the maximum amplitude? $\omega_0 = \sqrt{2}$, $\omega = 1$

$$A = \frac{F}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\eta\omega)^2}} = \frac{1}{\sqrt{1 + 9}} = \frac{1}{\sqrt{10}} = \frac{1}{\sqrt{10}}$$

$$\text{Or } A = \left| \frac{1 - 3i}{10} \right| = \frac{1}{10} |1 - 3i| = \frac{1}{10} \sqrt{10} = \frac{1}{\sqrt{10}}$$

If we want to blow up the system, what forcing function V should we choose?

From above, we know that $\omega = \sqrt{\omega_0^2 - 2\eta^2}$ maximizes amplitude

Let's write our ODE in appropriate form:

$$\ddot{I} + 3\dot{I} + 2I = e^{it}$$

$$\ddot{x} + 2\eta\dot{x} + \omega_0^2 x = f(t)$$

$$\text{So } \eta = \frac{3}{2} \text{ and } \omega_0 = \sqrt{2}$$

$$\omega = \sqrt{2 - \frac{9}{2}} = \sqrt{-\frac{5}{2}}$$

But ω is imaginary, so there is no real frequency we could choose to blow up the system.

The resistance in the system is high enough that no frequency gets magnified.